

**ECE 469 HDL**  
**Project 2, Part 1**  
**Tamanna Ravi Rupani**  
**UIN: 665679988**  
**MIPS**



1. A completed version of Table 1.

cycle	reset	pc	instr	branch	srca	srcb	alu out	zero	pcsrc	write data	mem write	read data
1	1	00	addi \$2, \$0,5 20020005	0	0	5	5	0	0	0	0	x
2	0	04	addi \$3, \$0,12 2003000c	0	0	C	c	0	0	0	0	x
3	0	08	addi \$7, \$3, -9 2067fff7	0	C	-9	3	0	0	0	0	x
4	0	0C	or \$4, \$7, \$2 00e220225	0	3	5	7	0	0	0	0	x
5	0	10	and \$5, \$3, \$4 00642824	0	C	7	4	0	0	0	0	x
6	0	14	add \$5, \$5, \$4 00a42820	0	4	7	b	0	0	0	0	x
7	0	18	beq \$5, \$7, end 10a7000a	1	B	3	8	0	0	0	0	x
8	0	1C	slt \$4, \$3, \$4 0064202a	0	C	7	0	1	0	0	0	x
9	0	20	beq \$4, \$0, around 10800001	1	0	0	0	1	1	0	0	x
	0	24	addi \$5, \$0,0 20050000									
10	0	28	slt \$4, \$7, \$2 00e2202a	0	3	5	1	0	0	0	0	x
11	0	2C	add \$7, \$4, \$5 00853820	0	1	B	c	0	0	0	0	X
12	0	30	sub \$7, \$7, \$2 00e23822	0	C	5	7	0	0	0	0	X
13	0	34	sw \$7,68(\$3) ac670044	0	C	[80]	[80] = 7	0	0	7	1	X
14	0	38	lw \$2,80(\$0) 8c020050	0	0	[80]	[80]	0	0	0	0	7
15	0	3C	j end 08000011	0	X	X	x	x	x	0	0	X
	0	40	addi \$2, \$0,1 20020001									
16	0	44	sw \$2,84(\$0) ac020054	0	0	[84]	[84] =7	0	0	7	1	X

2. An image of the simulation waveforms showing correct operation of the unmodified processor. Does it write the correct value to address 84?

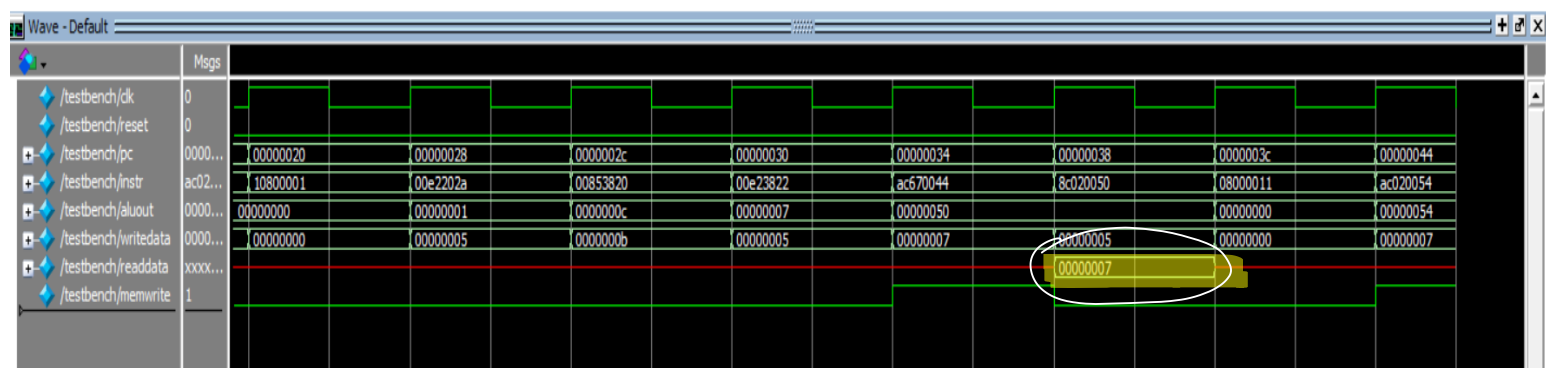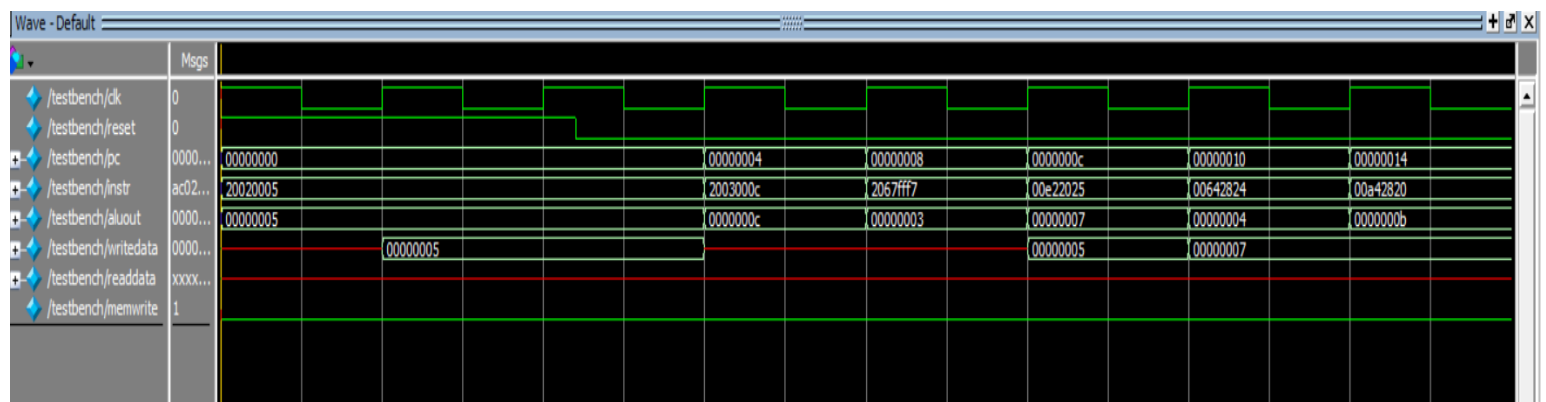
**Yes, the output 7 is successfully written to address 84 and the simulation is successful.**

```
# ** Warning: (vsim-WLF-5000) WLF file currently in use: vsim.wlf
# File in use by: taman Hostname: DESKTOP-POIKV0U ProcessID: 5144
# Attempting to use alternate WLF file ".\wlft2zj6g6".
# ** Warning: (vsim-WLF-5001) Could not open WLF file: vsim.wlf
# Using alternate file: .\wlft2zj6g6
VSIM6> run
# Simulation succeeded
# ** Note: $stop : C:/intelFPGA/17.1/testbench12.sv(24)
# Time: 175 ps Iteration: 1 Instance: /testbench
# Break in Module testbench at C:/intelFPGA/17.1/testbench12.sv line 24
VSIM 7>
```




3. Marked up versions of the datapath schematic and decoder tables that adds the ori and bne instructions

*Marked up version for ori*

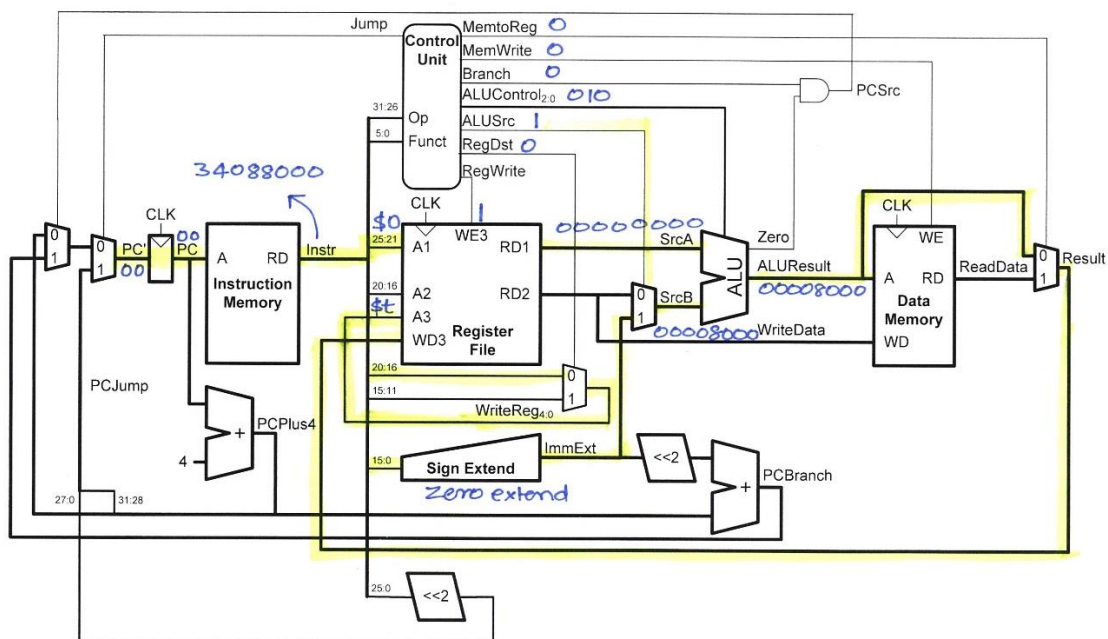

Single-cycle MIPS processor

*Marked up version for bne*

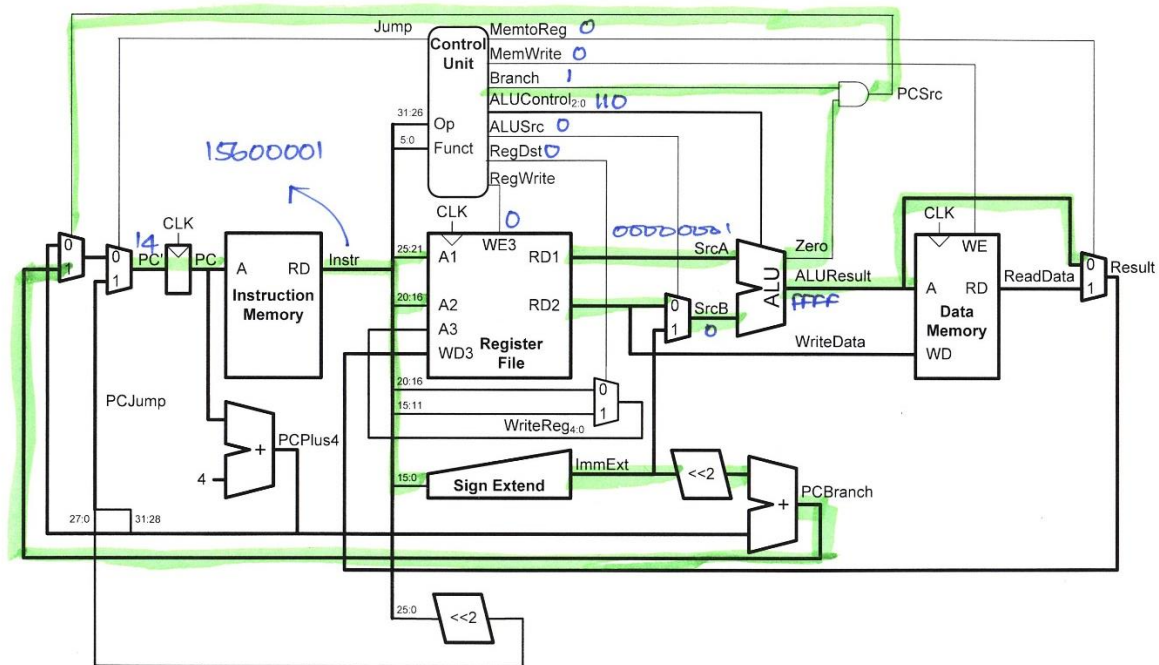

Single-cycle MIPS processor

### Extended functionality- Main Decoder:

Instruction	OP <sub>5:0</sub>	RegWrite	RegDst	AluSrc	Branch	MemWrite	MemtoReg	AluOP <sub>1:0</sub>	Jump
R-type	000000	1	1	0	0	0	0	10	0
Lw	100011	1	0	1	0	0	1	00	0
Sw	101011	0	X	1	0	1	X	00	0
Beq	000100	0	X	0	1	0	X	01	0
Addi	001000	1	0	1	0	0	0	00	0
J	000010	0	X	X	X	0	X	XX	1
Ori	001101	1	0	1	X	0	0	10	0
Bne	000101	0	X	0	1	0	X	01	0

### Extended functionality. ALU Decoder

ALUOp <sub>1:0</sub>	Meaning
00	Add
01	Subtract
10	Look at Funct field
11	n/a

4. Your SystemVerilog code for your modified MIPS computer (including ori and bne functionality) with the changes highlighted and commented in the code.

### SYSTEM VERILOG CODE FOR MODIFIED MIPS PROCESSOR

```
module top(input logic clk, reset,
           output logic [31:0] writedata, aluout,
           output logic memwrite,
           output logic [31:0] pc, instr, readdata);
    mips mips(clk, reset, pc, instr, memwrite, aluout, writedata, readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, aluout, writedata, readdata);

endmodule

module dmem(input logic clk, we,
            input logic [31:0] a, wd,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];
    assign rd=RAM[a[31:2]];

    always_ff @(posedge clk)
    if (we) RAM[a[31:2]] <= wd;

endmodule
```

```
endmodule
```

```
module imem(input logic [5:0] a,  
            output logic [31:0] rd);  
  
    logic [31:0] RAM[63:0];  
    initial $readmemh("C:/intelFPGA/17.1/memfile2.dat", RAM);  
    assign rd=RAM[a];  
endmodule
```

```
module mips(input logic clk, reset,  
            output logic [31:0] pc,  
            input logic [31:0] instr,  
            output logic memwrite,  
            output logic [31:0] aluout, writedata,  
            input logic [31:0] readdata);
```

```
    logic memtoreg, alusrc, regdst, regwrite, jump, pcsrc, zero;  
    logic [2:0] alucontrol;
```

```
    controller c(instr[31:26], instr[5:0], zero, aluout, memtoreg, memwrite, pcsrc, alusrc, regdst, regwrite, jump,  
    alucontrol); //aluout is added her for the modified code
```

```
    datapath dp(clk, reset, instr[31:26], memtoreg, pcsrc, alusrc, regdst, regwrite, jump, alucontrol, zero, pc,  
    instr, aluout, writedata, readdata);
```

```
endmodule
```

```
module controller(input logic [5:0] op, funct,  
                  input logic zero,  
                  input logic [31:0] aluout, //This part is added for modification  
                  output logic memtoreg, memwrite,  
                  output logic pcsrc, alusrc,  
                  output logic regdst, regwrite,  
                  output logic jump,  
                  output logic [2:0] alucontrol);
```

```
    logic [1:0] aluop;  
    logic branch;  
    logic fun1;  
    logic z;  
    logic [5:0] fun2;
```

```
//This part is added for modification
```

```
always_comb
```

```
if ( op === 6'b001101)
```

```
fun1 = 1;
else
fun1 = 0;
```

```
always_comb
if ( fun1 === 1'b0 )
fun2 = funct;
else
fun2 = 6'b100101;
```

```
maindec md(op, memtoreg, memwrite, branch, alusrc, regdst, regwrite, jump, aluop);
aludec ad(fun2, aluop, alucontrol);
```

```
//This part is added for modification
```

```
always_comb
if ( op === 6'b000101 & aluout !== 32'b00000000000000000000000000000000 )
z = 1'b1;
else z = zero;
```

```
assign pcsrc = branch & z;
```

```
endmodule
```

```
module maindec(input logic [5:0] op,
               output logic memtoreg, memwrite,
               output logic branch, alusrc,
               output logic regdst, regwrite,
               output logic jump,
               output logic [1:0] aluop);
```

```
logic [8:0] controls;
```

```
assign {regwrite, regdst, alusrc, branch, memwrite, memtoreg, jump, aluop}=controls;
```

```
always_comb
```

```
case(op)
```

```
6'b000000: controls <= 9'b110000010; // RTYPE
```

```
6'b100011: controls <= 9'b101001000; // LW
```

```
6'b101011: controls <= 9'b001010000; // SW
```

```
6'b000100: controls <= 9'b000100001; // BEQ
```

```
6'b000101: controls <= 9'b000100001; // BNE
```

```
6'b001000: controls <= 9'b101000000; // ADDI
```

```
6'b001101: controls <= 9'b101000010; // ORI
```

```
6'b000010: controls <= 9'b000000100; // J
```

```
default: controls <= 9'bxxxxxxxx; // illegal op
```

```
endcase
```

```

endmodule
module aludec(input logic [5:0] funct,
              input logic [1:0] aluop,
              output logic [2:0] alucontrol);

always_comb
case(aluop)
2'b00: alucontrol <= 3'b010; // add (for lw/sw/addi)
2'b01: alucontrol <= 3'b110; // sub (for beq)
default: case(funct) // R-type instructions
        6'b100000: alucontrol <= 3'b010; // add
        6'b100010: alucontrol <= 3'b110; // sub
        6'b100100: alucontrol <= 3'b000; // and
        6'b100101: alucontrol <= 3'b001; // or
        6'b101010: alucontrol <= 3'b111; // slt
        default: alucontrol <= 3'bxxx; // ???
      endcase
endcase

```

```

endmodule

```

```

module datapath(input logic clk, reset,
                input logic [5:0] opcode,
                input logic memtoreg, pcsrc,
                input logic alusrc, regdst,
                input logic regwrite, jump,
                input logic [2:0] alucontrol,
                output logic zero,
                output logic [31:0] pc,
                input logic [31:0] instr,
                output logic [31:0] aluout, writedata,
                input logic [31:0] readdata);

```

```

logic [4:0] writereg;
logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
logic [31:0] signimm, signimmsh;
logic [31:0] srca, srebr;
logic [31:0] result;
logic fun1;

```

```

flopr #(32) pcreg(clk, reset, pcnext, pc);
adder pcadd1(pc, 32'b100, pcplus4);
sl2 immsh(signimm, signimmsh);
adder pcadd2(pcplus4, signimmsh, pcbranch);
mux2 #(32) pcbrmux(pcplus4, pcbranch, pcsrc, pcnextbr);
mux2 #(32) pcmux(pcnextbr, {pcplus4[31:28], instr[25:0], 2'b00}, jump, pcnext);

```

```

regfile rf(clk, regwrite, instr[25:21], instr[20:16], writereg, result, srca, writedata);
mux2 #(5) wrmux(instr[20:16], instr[15:11], regdst, writereg);
mux2 #(32) resmux(aluout, readdata, memtoreg, result);

```

```

//This part is added for modification

```

```

always_comb
if ( opcode === 6'b001101)
fun1 = 1;
else
fun1 = 0;

```

```

always_comb
if( fun1 === 1'b1)
signimm={ 16'b0, instr[15:0]};
else
signimm={{ 16{instr[15]}}, instr[15:0]};

```

```

//signext se(instr[15:0], signimm);
mux2 #(32) srcbmux(writedata, signimm, alusrc, srcb);
alu alu(srca, srcb, alucontrol, aluout, zero);

```

```

endmodule

```

```

module alu(input logic [31:0] a, b,
          input logic [2:0] F,
          output logic [31:0] Y,
          output logic zero);
logic [31:0] S , B;

```

```

assign B = F[2]? ~b:b;

```

```

assign S = a + B + F[2];

```

```

always_comb
case(F[1:0])
2'b00 : Y = a & B;
2'b01 : Y = a | B;
2'b10 : Y = S;
2'b11 : Y = {31'b0,S[31]};
endcase

```

```

always_comb
if ( Y === 32'b0)
zero = 1;

```



```

else zero =0;
endmodule

module regfile(input logic clk,
               input logic we3,
               input logic [4:0] ra1, ra2, wa3,
               input logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

    logic [31:0] rf[31:0];

    always_ff @(posedge clk)
    if (we3)
        rf[wa3] <= wd3;

    assign rd1=(ra1 !=0) ? rf[ra1] : 0;
    assign rd2=(ra2 !=0) ? rf[ra2] : 0;

endmodule

module adder(input logic [31:0] a, b,
             output logic [31:0] y);

    assign y=a+b;

endmodule

module sl2(input logic [31:0] a,
           output logic [31:0] y);

    assign y={ a[29:0], 2'b00};

endmodule

module flopr #(parameter WIDTH=8) (input logic clk, reset,
                                   input logic [WIDTH-1:0] d,
                                   output logic [WIDTH-1:0] q);

    always_ff @(posedge clk, posedge reset)
    if (reset) q <= 0;
    else q <= d;
endmodule

module mux2 #(parameter WIDTH=8) (input logic [WIDTH-1:0] d0, d1,
                                   input logic s,
                                   output logic [WIDTH-1:0] y);

    assign y=s ? d1 : d0;
endmodule

```

## TESTBENCH CODE FOR THE MODIFIED MIPS PROCESSORS

```
module testbenchmod();
logic clk; logic reset;
logic [31:0] writedata, aluout;
logic memwrite;
logic [31:0] pc, instr, readdata;
topmod dut (clk, reset, writedata, aluout, memwrite,pc, instr, readdata);
initial
begin
reset <= 1; # 22; reset <= 0;
end

always
begin
clk <= 1; # 5; clk <= 0; # 5;
end

always @(negedge clk)
begin
if (memwrite)
begin
if (aluout===84)
begin
$display("Simulation succeeded");
$stop;
end
else if (aluout !==80)
begin
$display("Simulation failed");
$stop;
end
end
end

end
endmodule
```



5. The contents of your memfile2.dat containing your test2 machine language code.

34088000  
20098000  
350A8001  
11090005  
0128582A  
15600001  
08000009  
01485022  
350800FF  
016A5820  
01484022  
AD680052

6. An image of the simulation waveforms showing correct operation of your modified processor on the new program. What address and data value are written by the sw instruction?

```
add wave -position insertpoint sim:/testbenchmod/*  
# ** Warning: (vsim-WLF-5000) WLF file currently in use: vsim.wlf  
#       File in use by: taman  Hostname: DESKTOP-POIKV0U  ProcessID: 5144  
#       Attempting to use alternate WLF file "./wlftdcj850".  
# ** Warning: (vsim-WLF-5001) Could not open WLF file: vsim.wlf  
#       Using alternate file: ./wlftdcj850  
VSIM 13> run  
# Simulation succeeded  
# ** Note: $stop      : C:/intelFPGA/17.1/testbenchmod.sv(24)  
#       Time: 125 ps  Iteration: 1  Instance: /testbenchmod  
# Break in Module testbenchmod at C:/intelFPGA/17.1/testbenchmod.sv line 24  
VSIM 14>
```

Project : hdlproject2	Now: 125 ps  Delta: 1
-----------------------	-----------------------

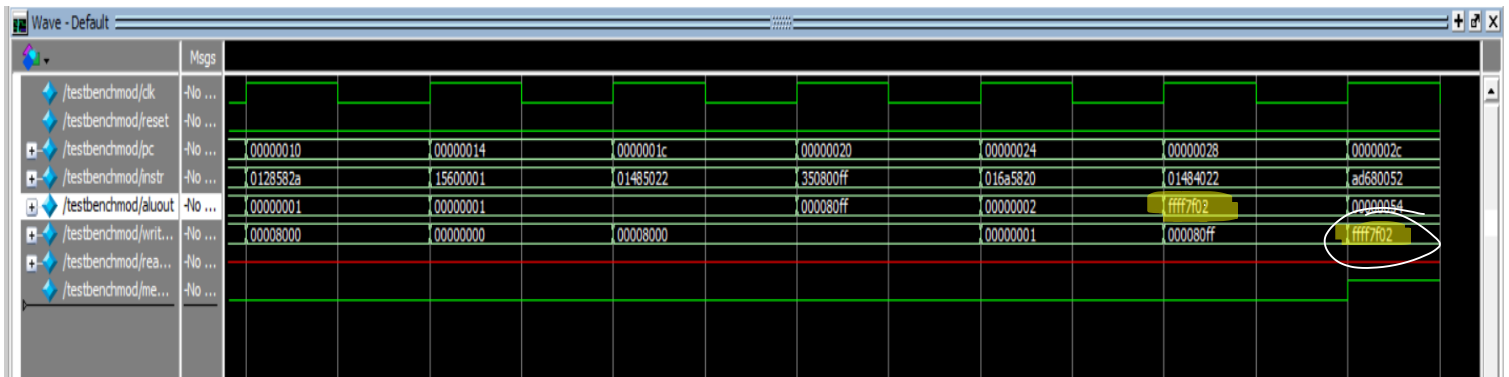 

**Address and data value are written by the sw instruction is,**

**Address: 00000084**

**Data: ffff7f02**

7. Workload report: How many hours have you spent on this part? Which activity takes the most significant amount of time? This will not affect your grade (unless omitted).


Activity	Time
Studying chapter 6 and 7, understanding MIPS concept	6 hours
Filling the table 1, decoder table, alu table	2 hours
Understanding the SystemVerilog code	2-3 hours
Execution of SystemVerilog code and debugging errors	3+ hours
Modifying new machine language code	2-3 hours
New SystemVerilog code for modified MIPS	2 hours
Execution of new modified code	2 hours
Quartus part	1 hour
Making the report	4 hours
Total time	24+ hours

The activity of executing and debugging the processor code takes the most amount of time, along with modifying the code for the new modified processor.


8. (extra credit) RTL view from Quartus' compilation result of your MIPS processor: before and after the modification. Can you identify the changes?

### Before Modification


Normal view

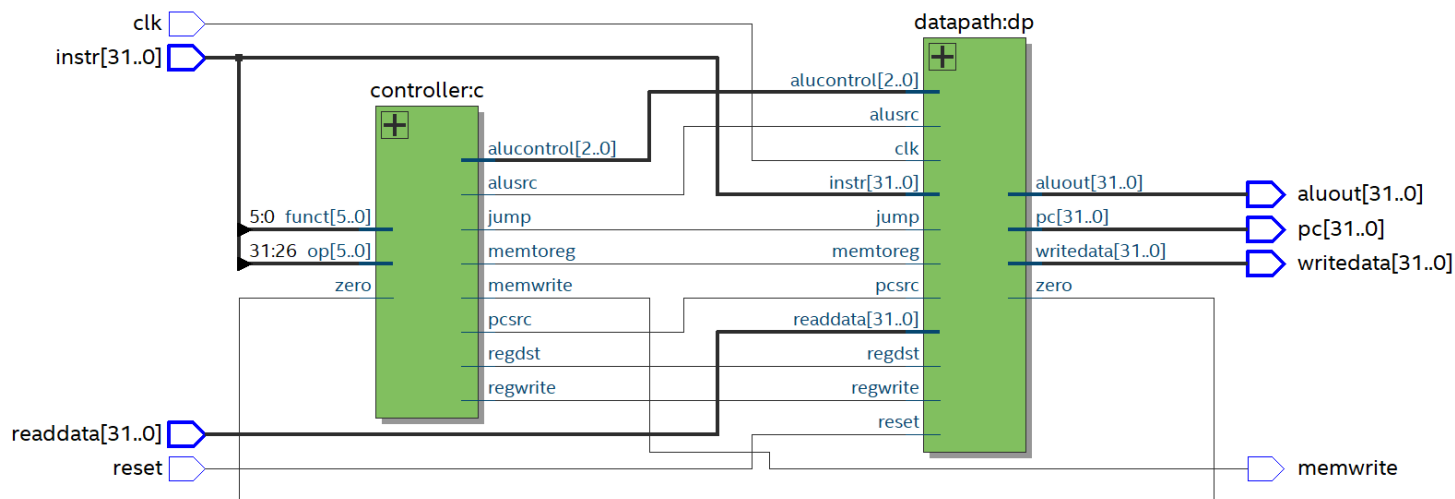


Inside controller:c

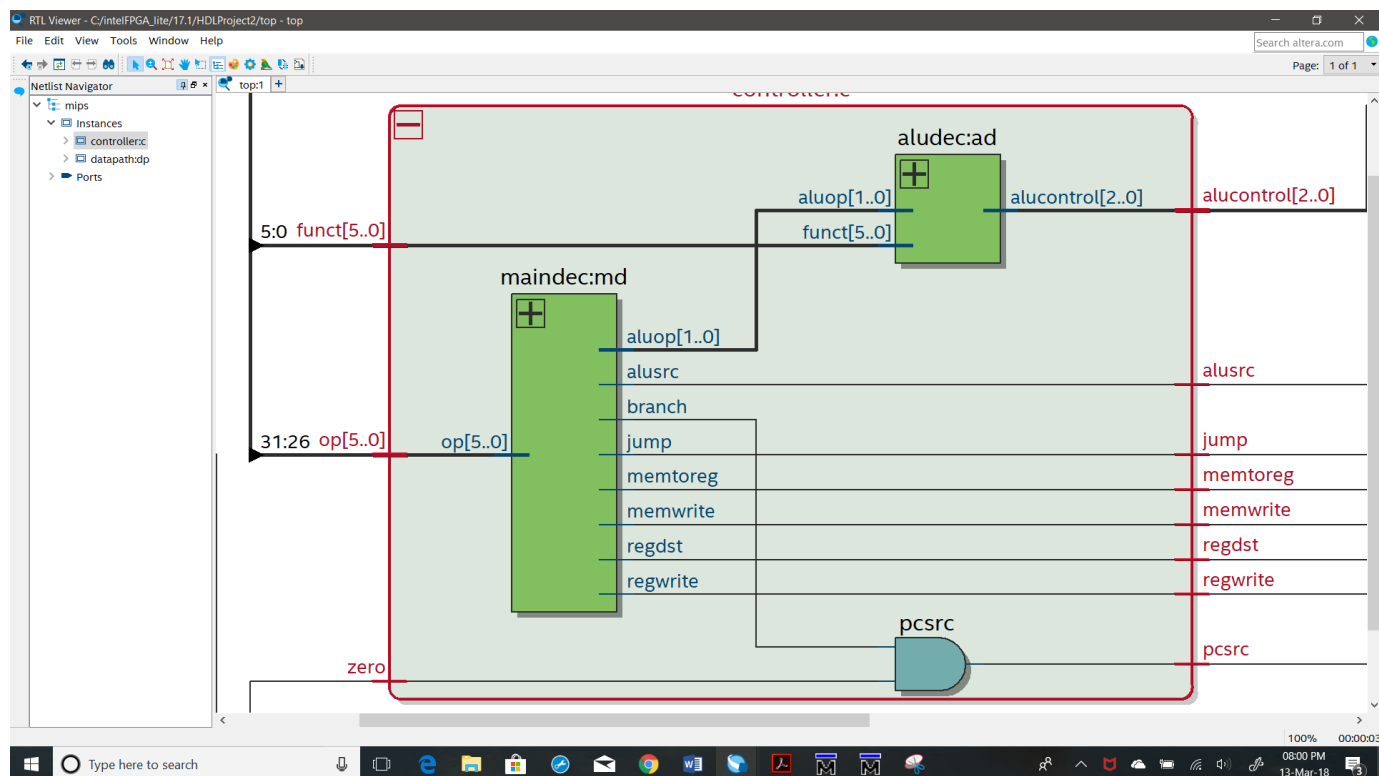


## Inside maindec:md

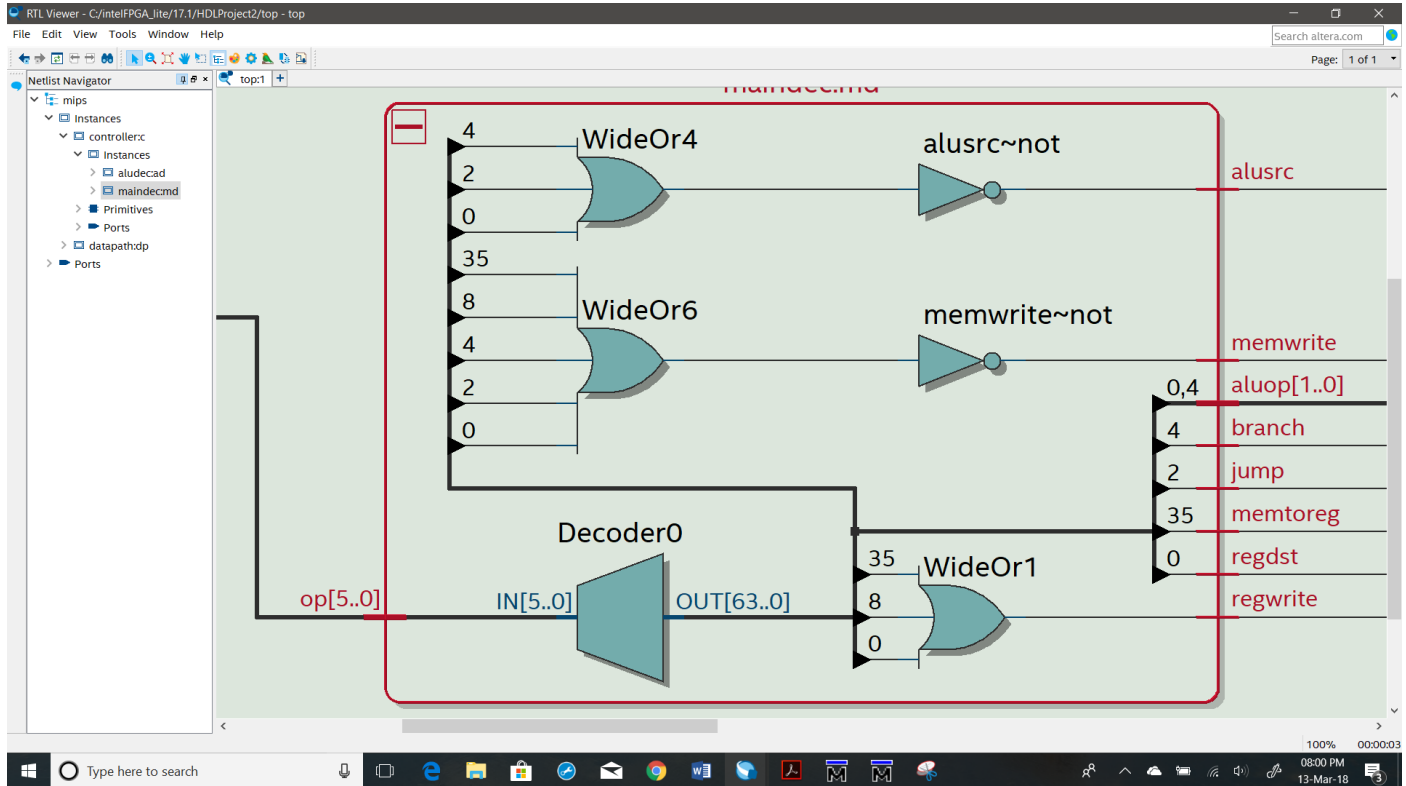


## Inside aludec:ad

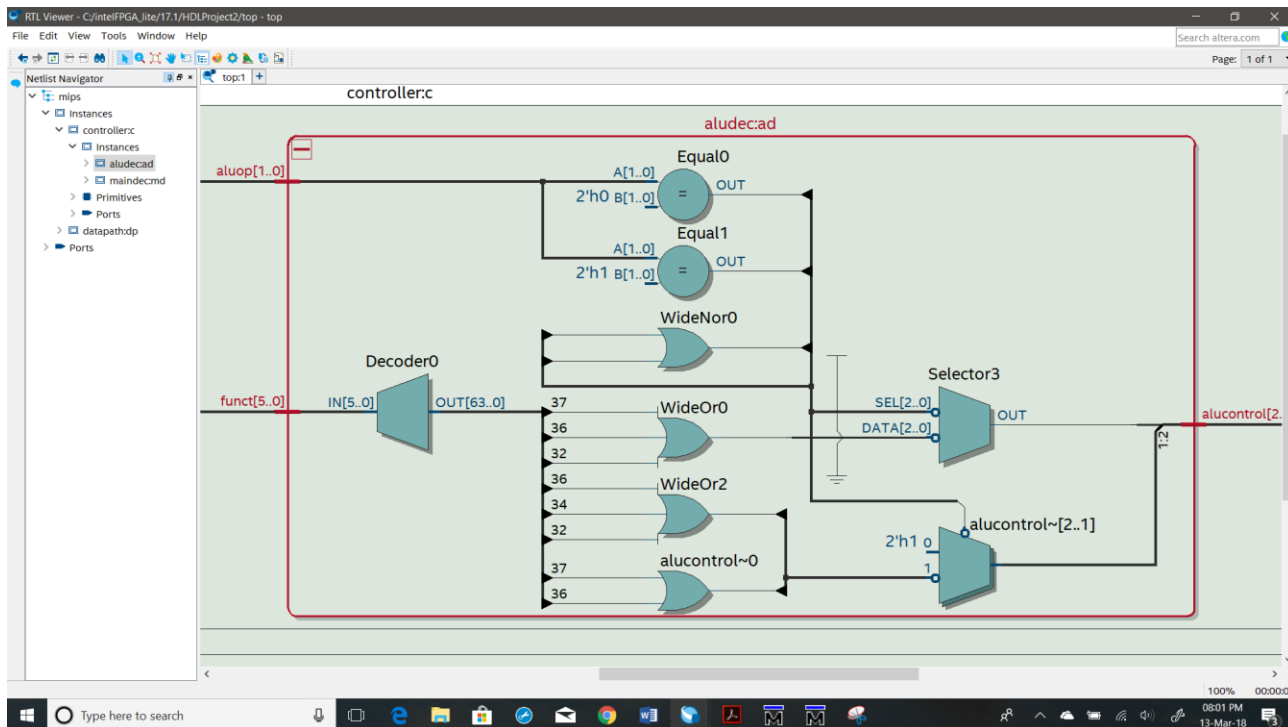


## Inside datapath:dp

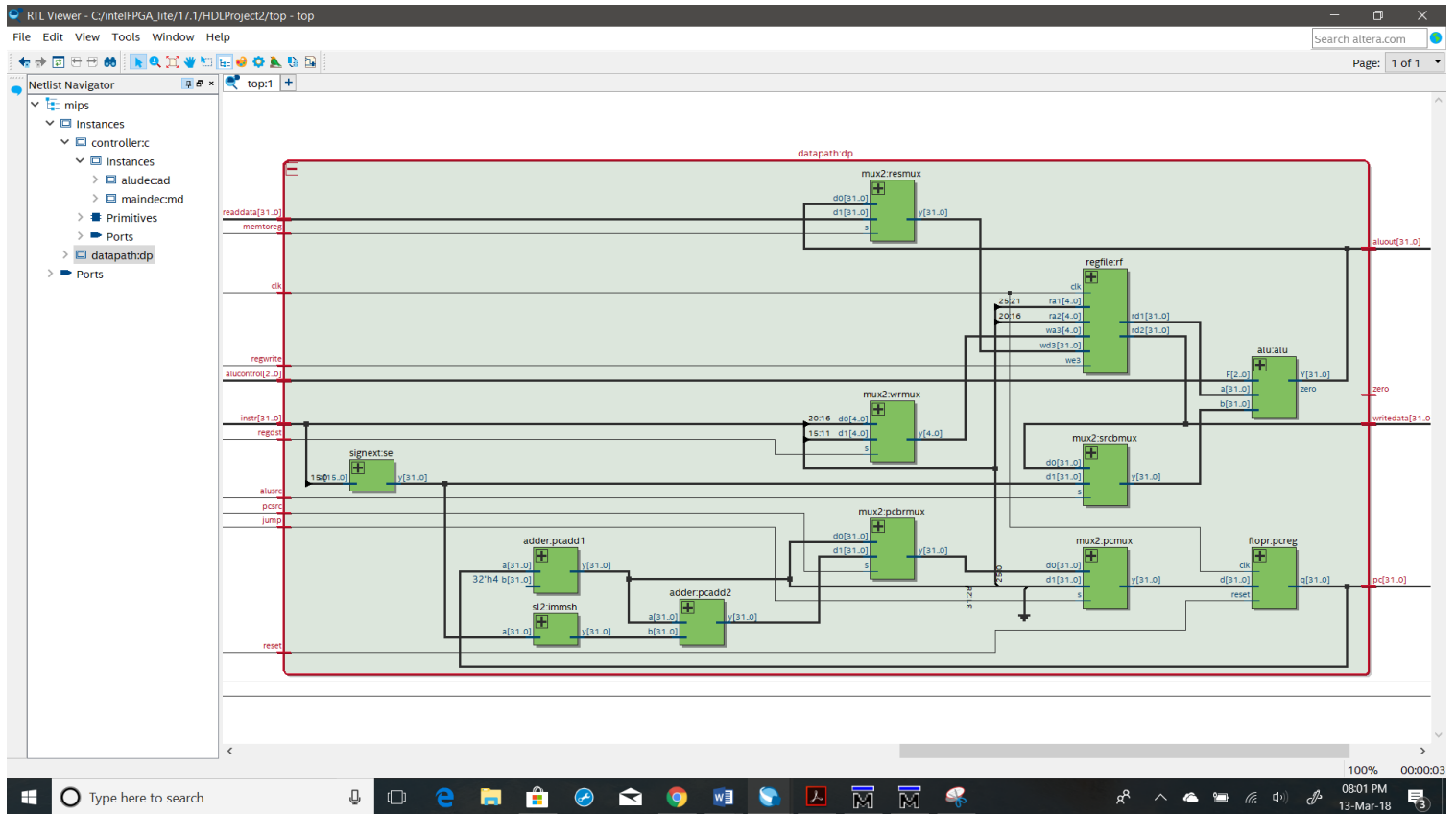



## Zoomed view inside datapath modules

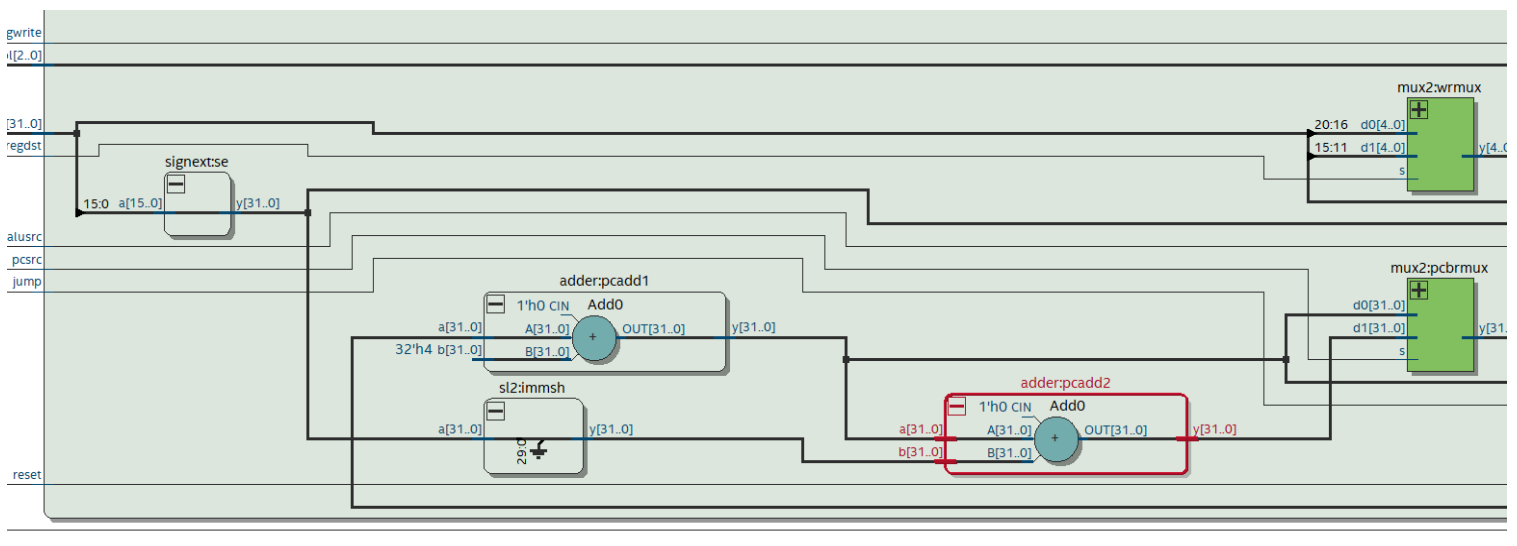

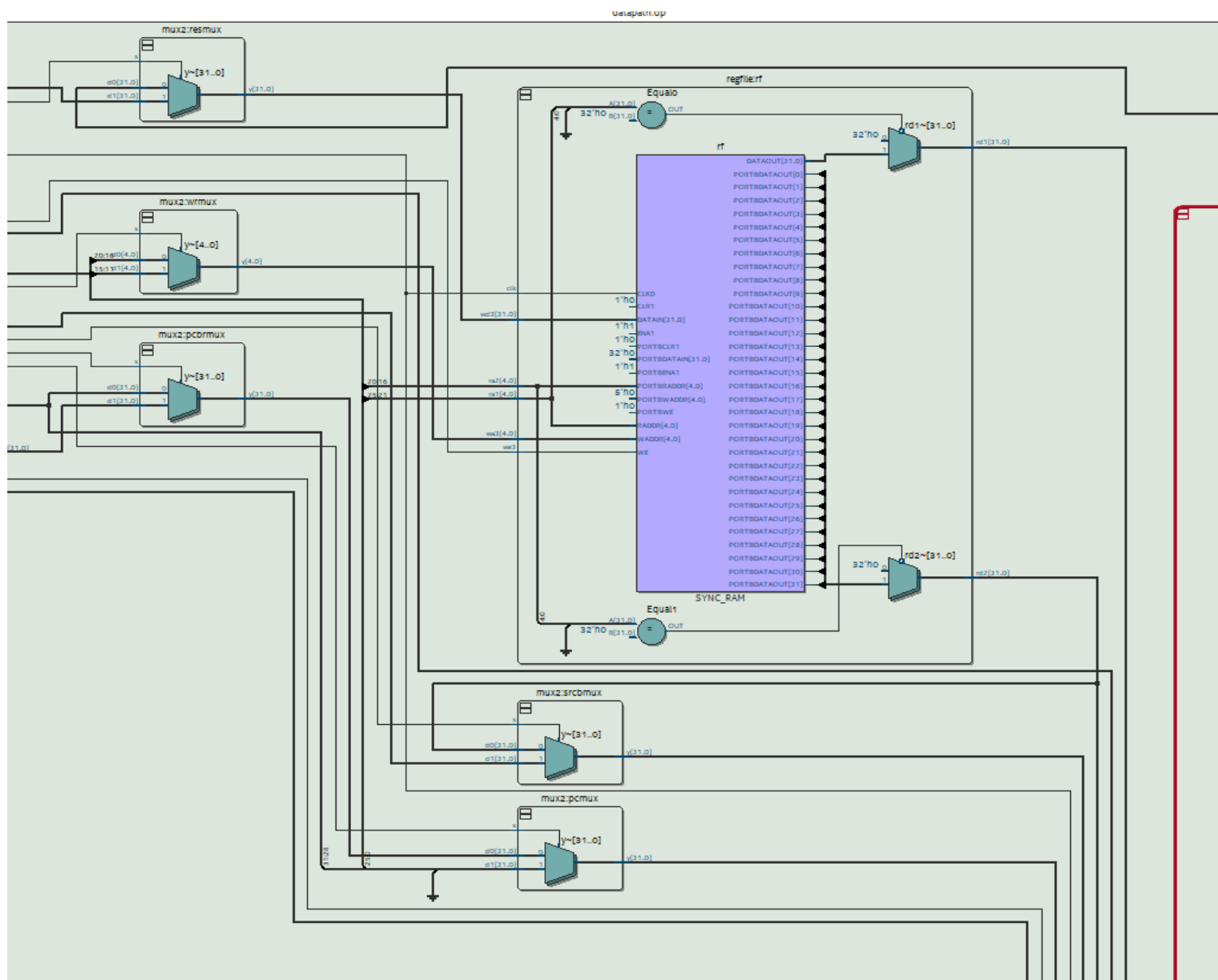





Inside alu

 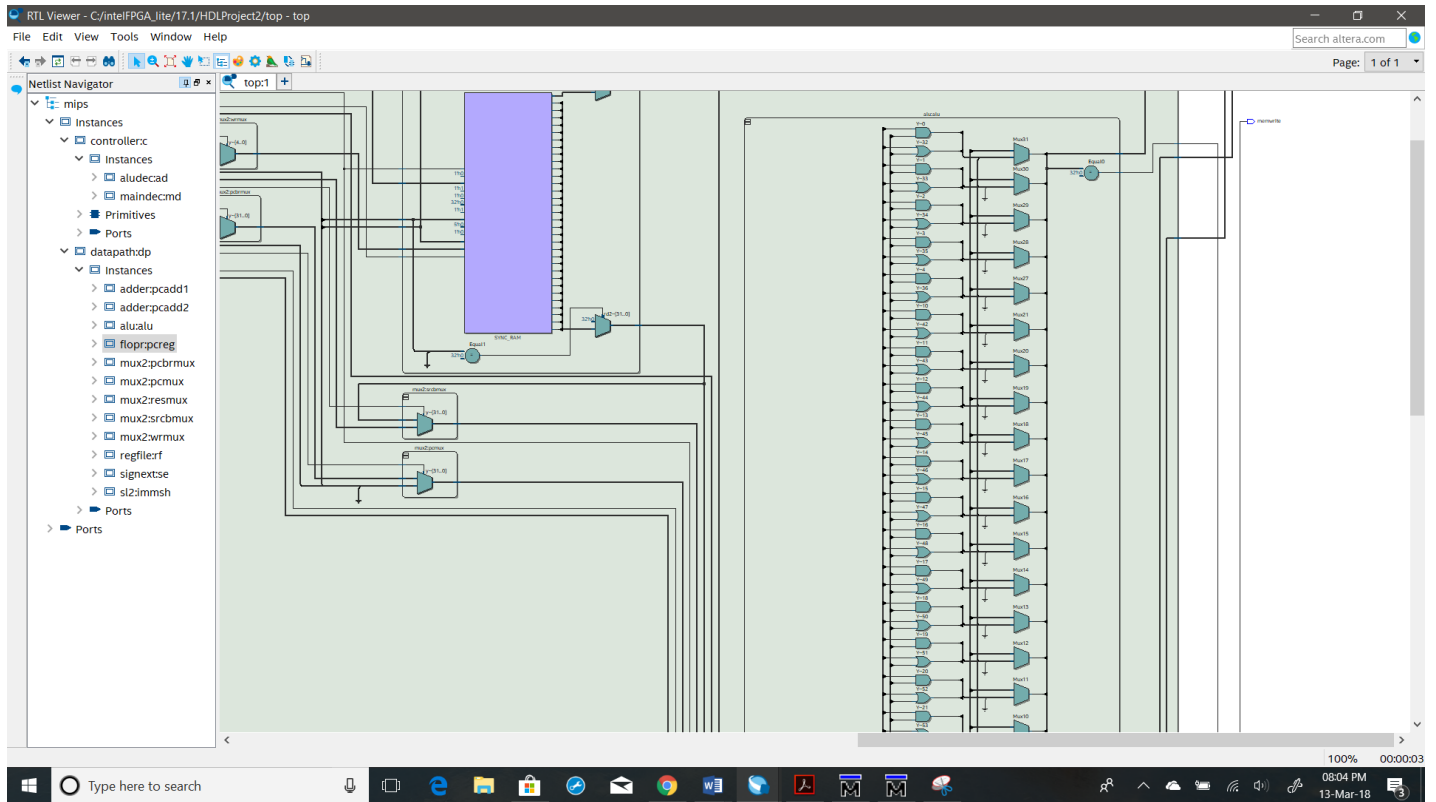

## After modification

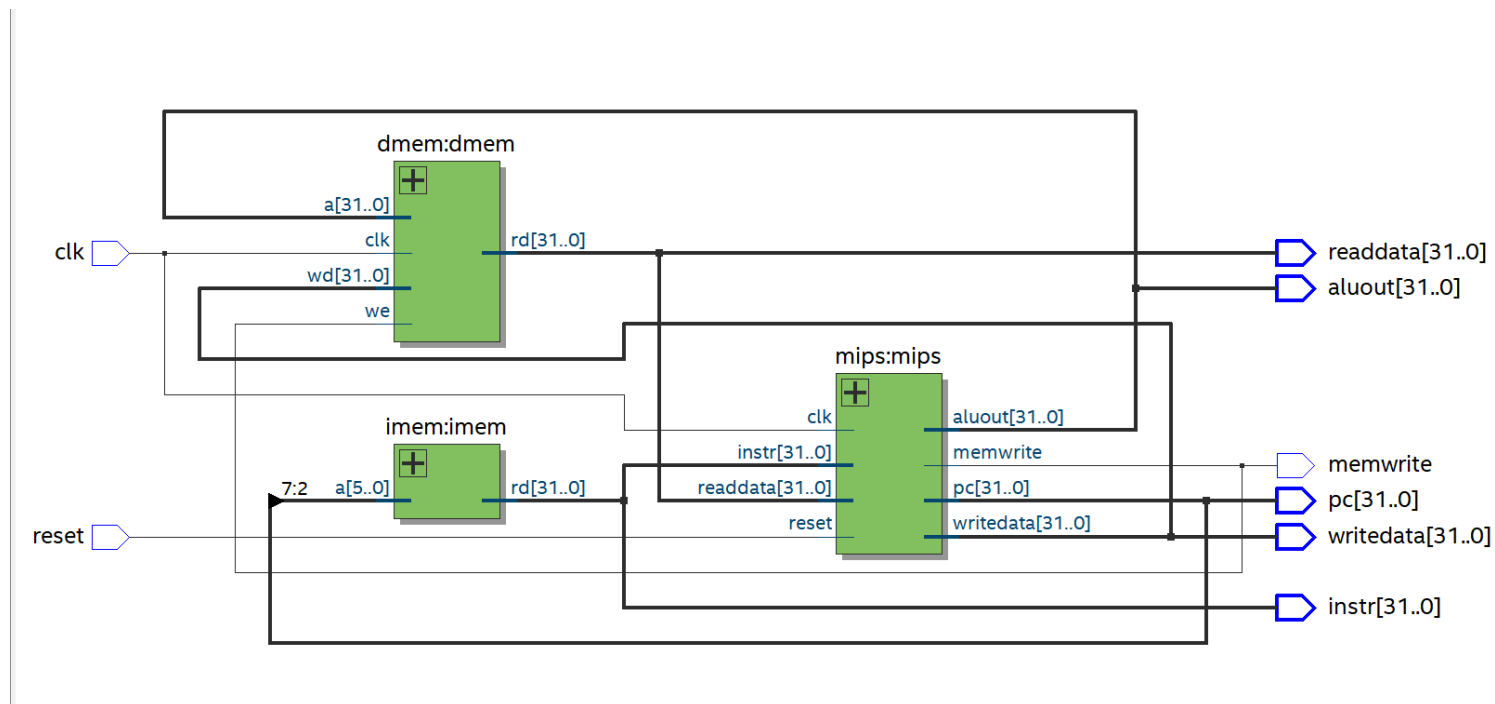


## Inside dmem

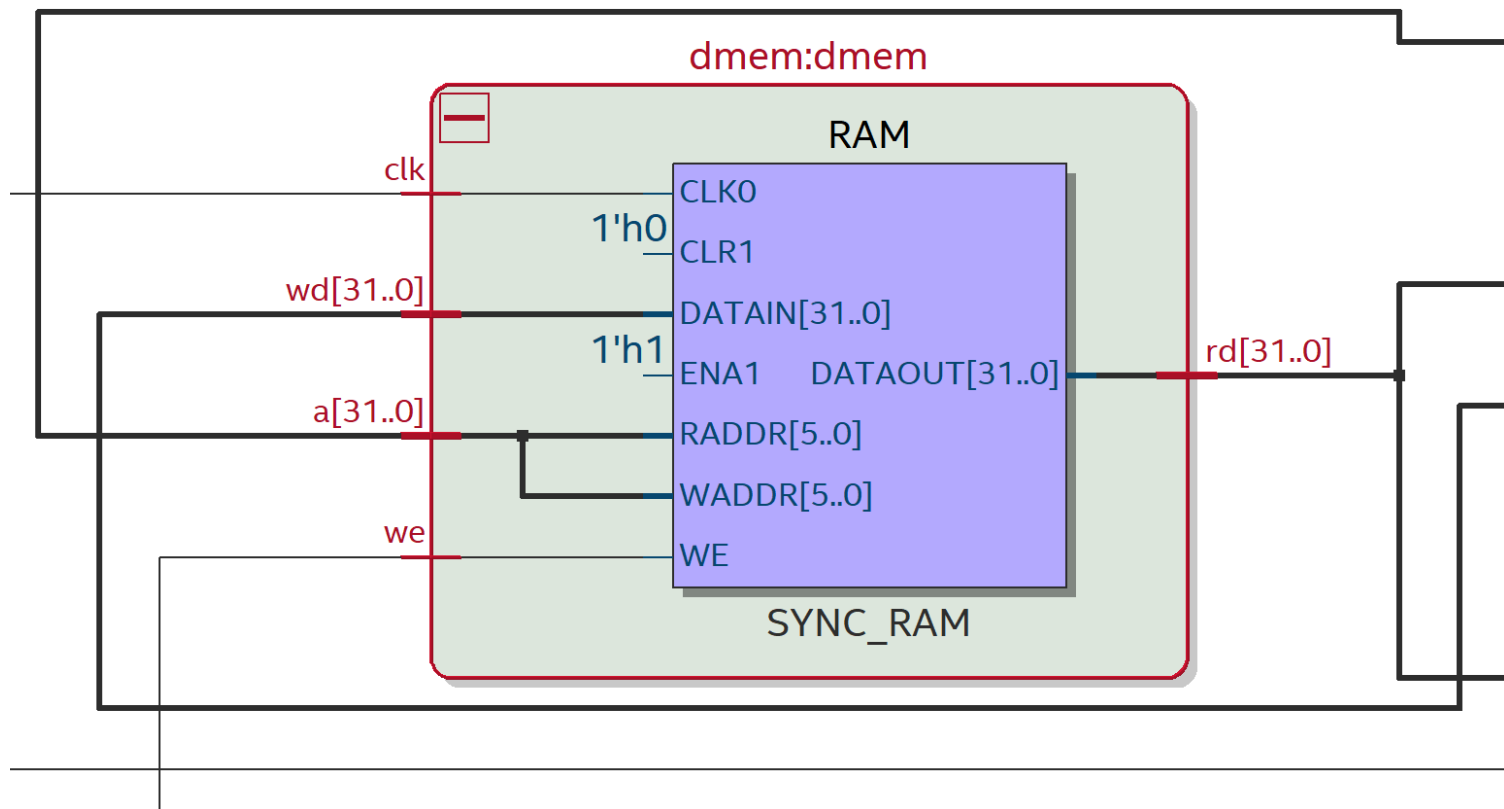








## Inside datapath

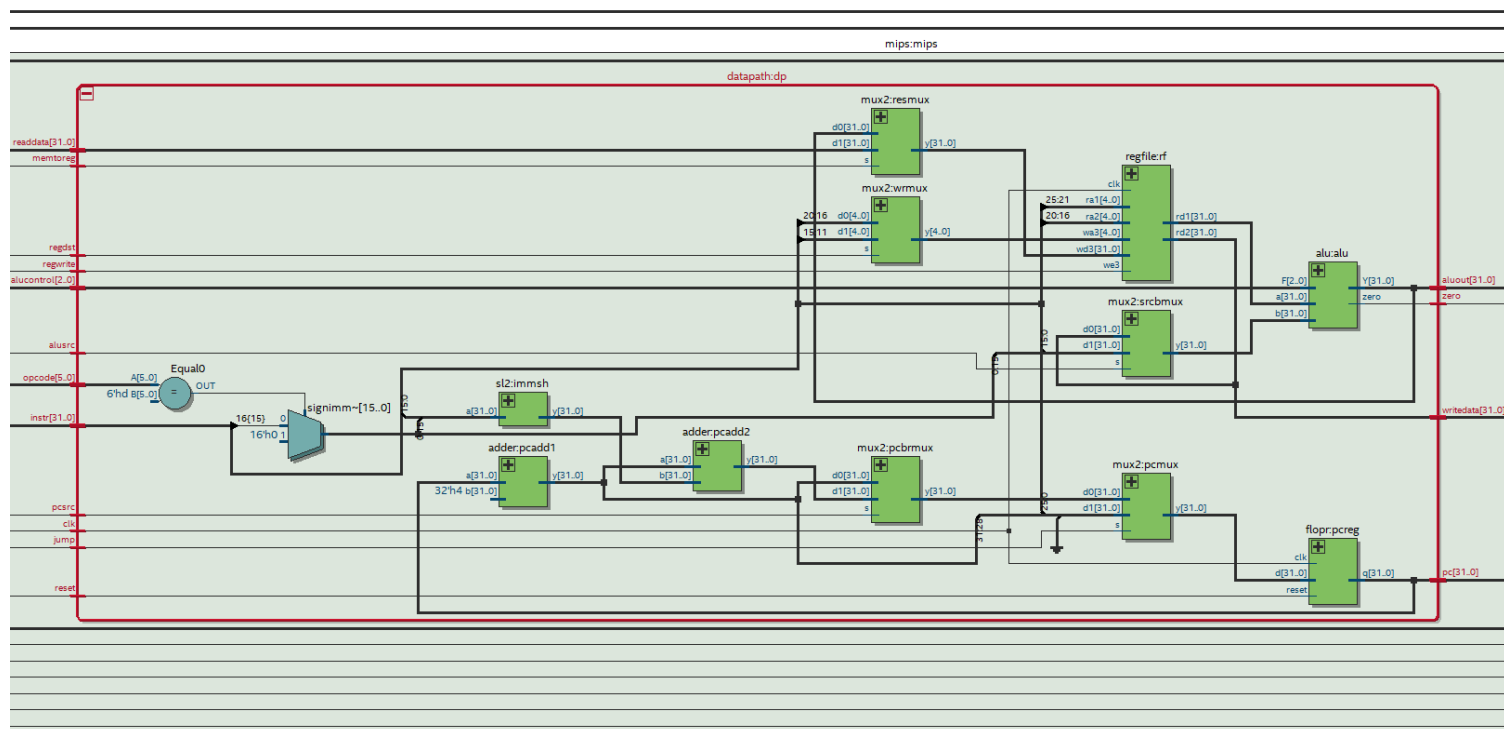


## Zoomed view inside the datapath

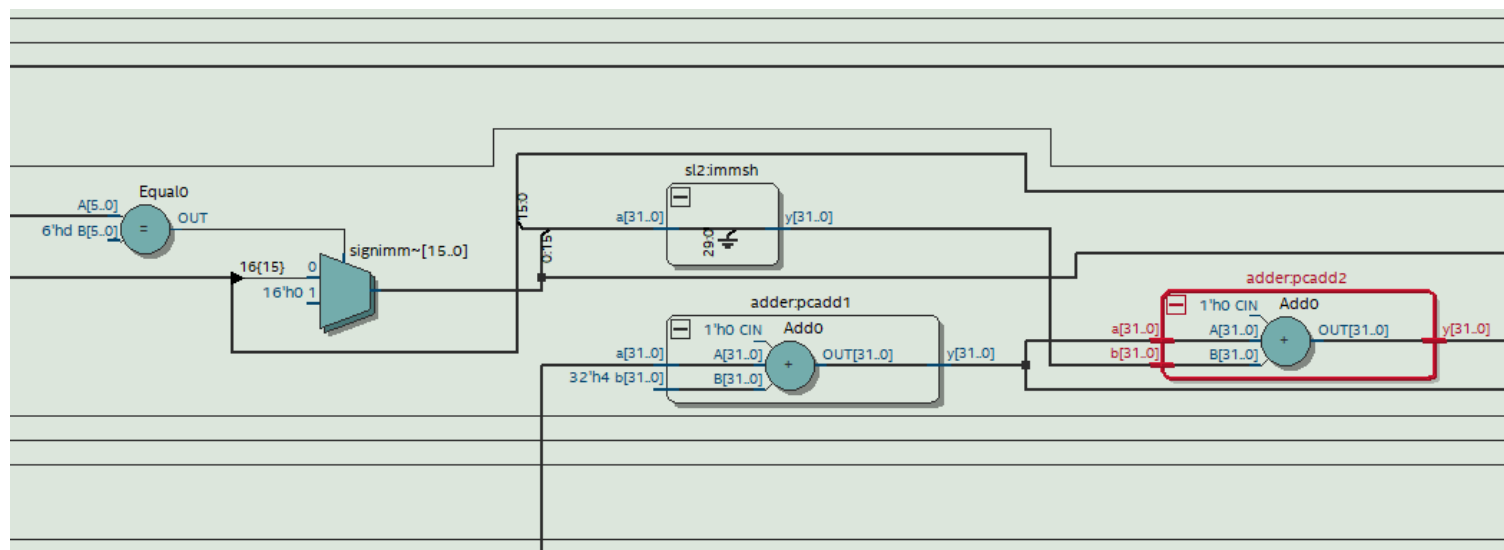

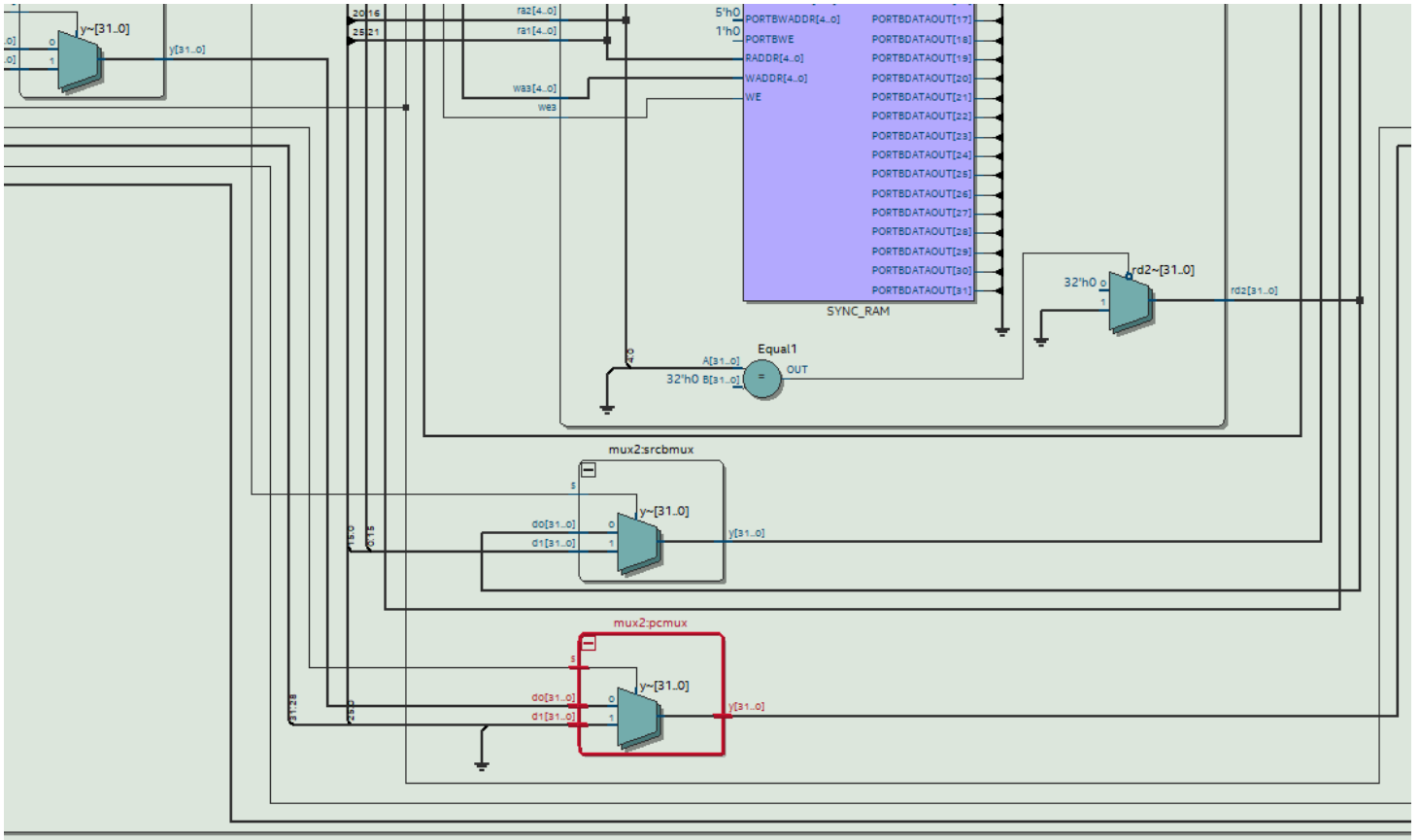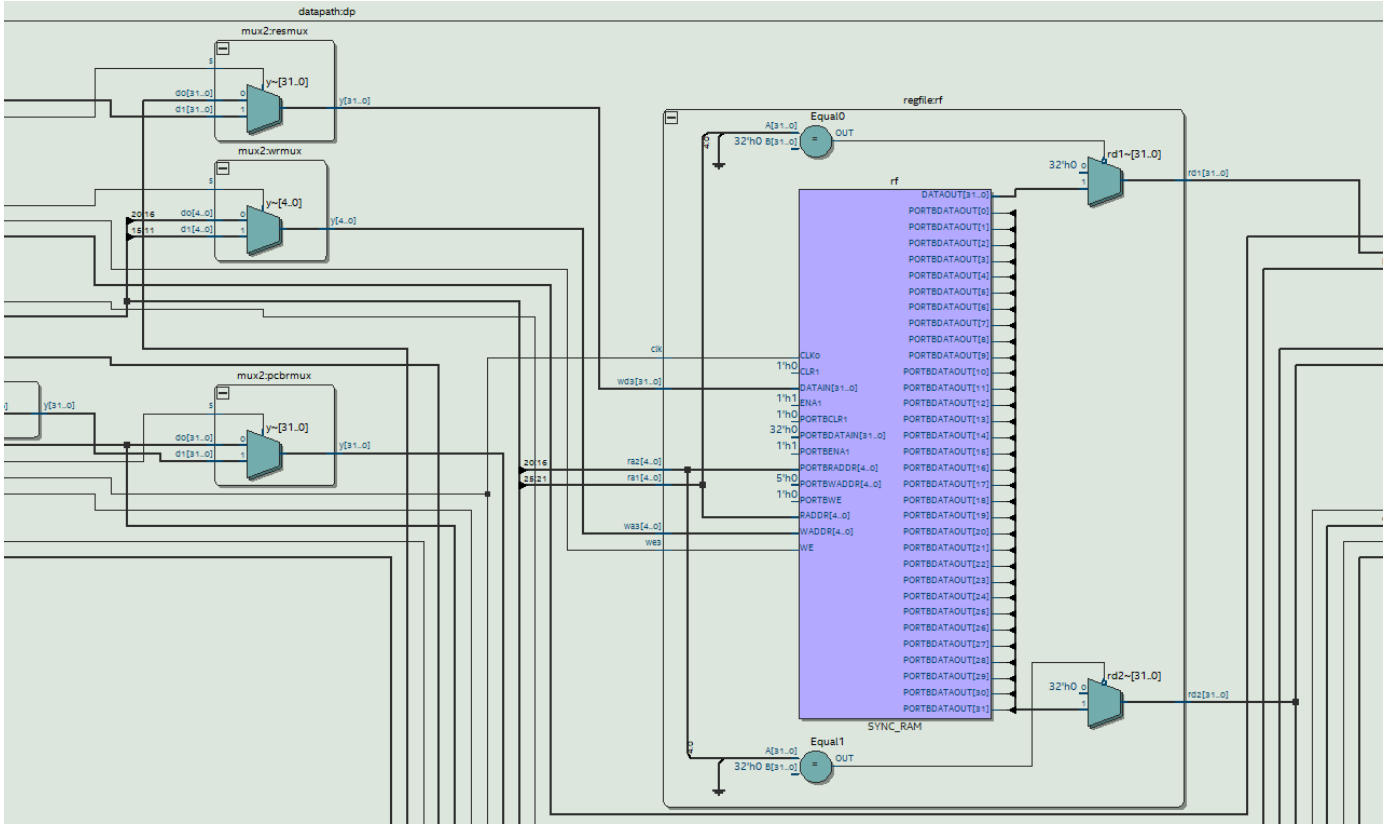


  

## Inside controller

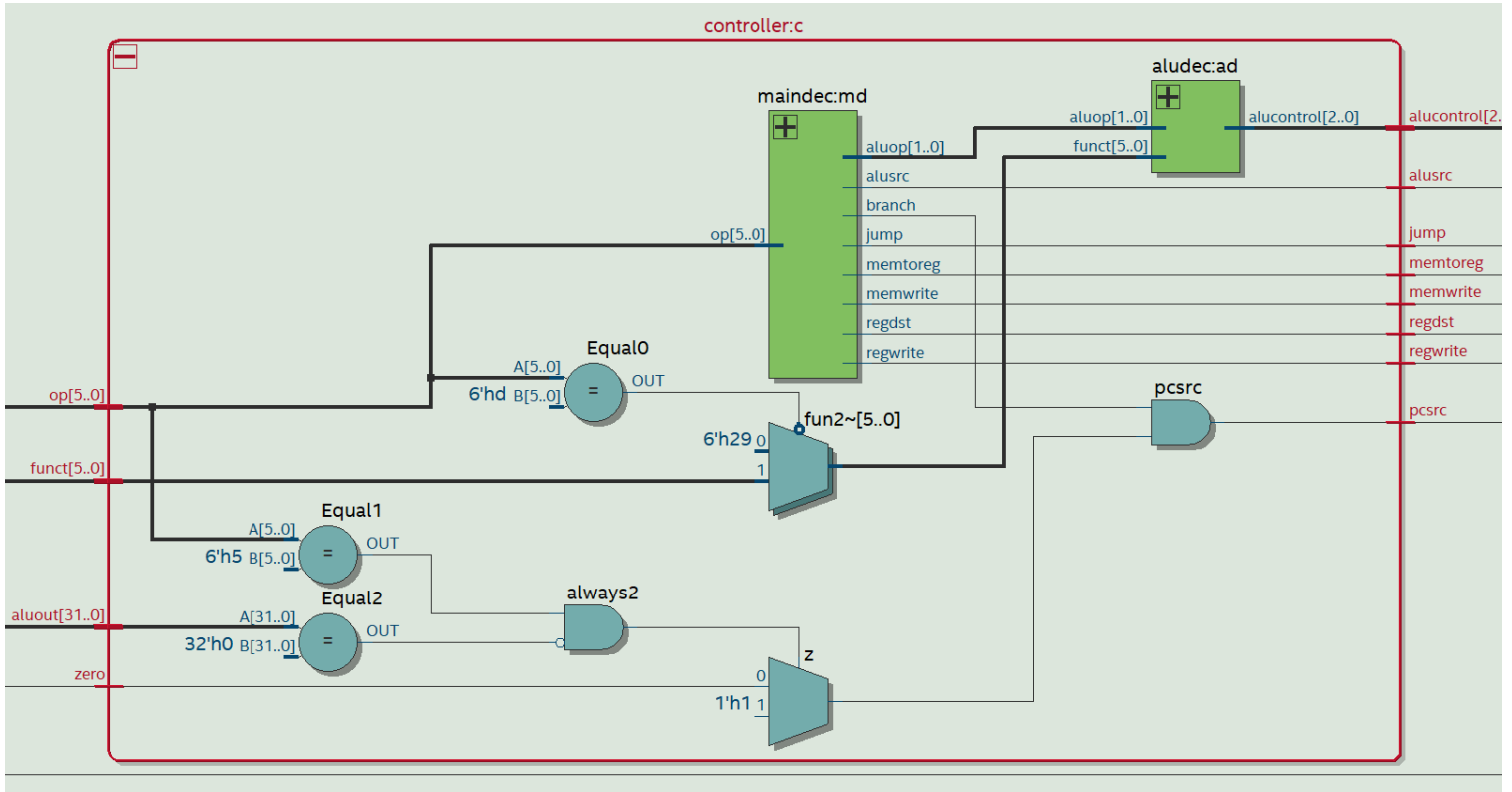

## Inside maindec and aludec

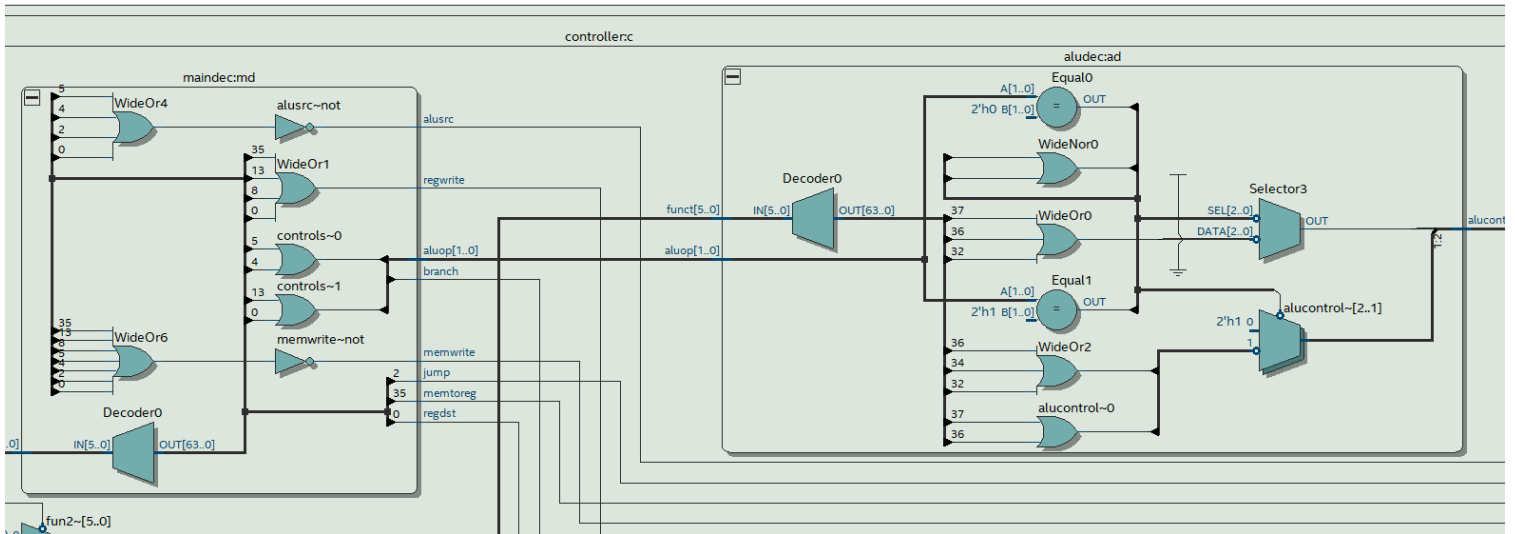

Changes identified are:

There is a change in the maindec module between the modified and unmodified code. The modified code has extra number of OR gates as control 0 and control 1.

Another change is in the aludec module. The modified aludec has changes in the positioning of the gates which changes the paths to be taken.

The basic working and the diagrammatic representation remains the same for both the MIPS processors, only that specific changes take place in sub-modules as states above.